

# Hardware System Design (Advanced Digital Systems Design)

4190.309A

2013 Spring Semester


## Power Supply Theory and Practice

**Naehyuck Chang**  
**Dept. of EECS/CSE**  
**Seoul National University**  
**[naehyuck@snu.ac.kr](mailto:naehyuck@snu.ac.kr)**




# Ideal versus real-world power supply

Why real power supplies are noisy?

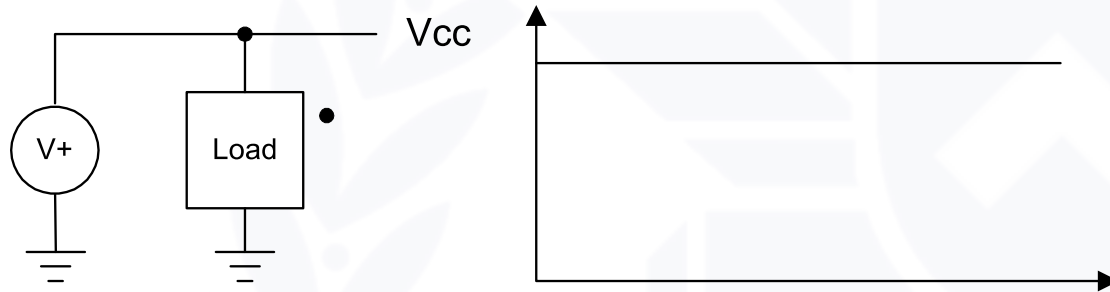

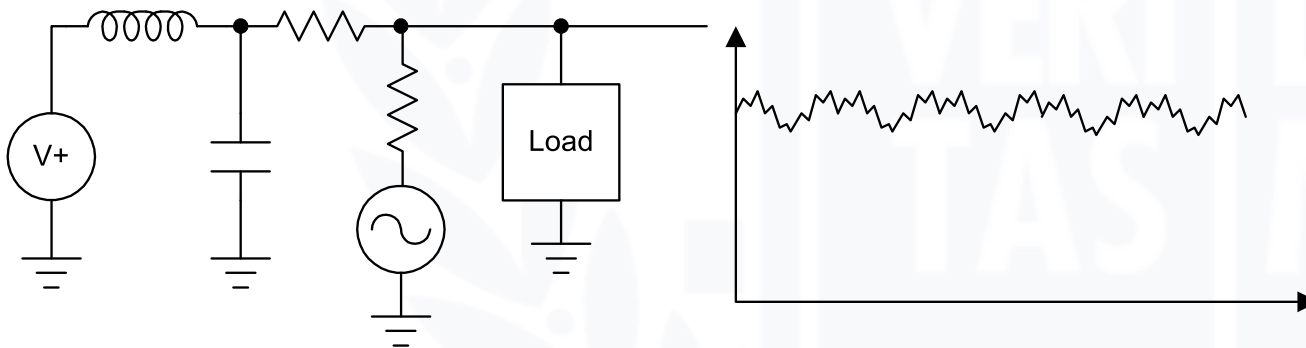a) Ideal power source: zero line impedance



b) Realistic power source: non-zero line impedance

# Good power supply

- Minimize power supply impedance
  - as much as possible.
- Power supply impedance
  - Resistive component
  - Inductive component

$$V_{drop} = iR + L \frac{di}{dt}$$

# Voltage drop:

$$V_{drop} = iR + L \frac{di}{dt}$$

- 20A current with DC resistance 0.05Ω
  - yields 1V drop.
  - TTL operating range is 4.75V to 5.25V
- 0.1A current change in 2ns with 500nH
  - yields 25V drop!
  - In practice, yields much less voltage drop since 500nH prevents 0.1A current change itself in 2ns.

# Reducing DC resistance


- Use low resistance materials: copper
- Use thick wire
- Reduce contact resistance
- Internal impedance (resistance) of a power supply is also important.

# Reducing inductance

- Use short wire.
- Make no bend or loop if possible.
- VCC is as important as GND.
- Use bypass capacitors.
- Wire thickness is not so important!
- If somebody fails in reducing inductance, he or she may suffer from ground bounce.


# Ground bounce

🌍 Earthquake!

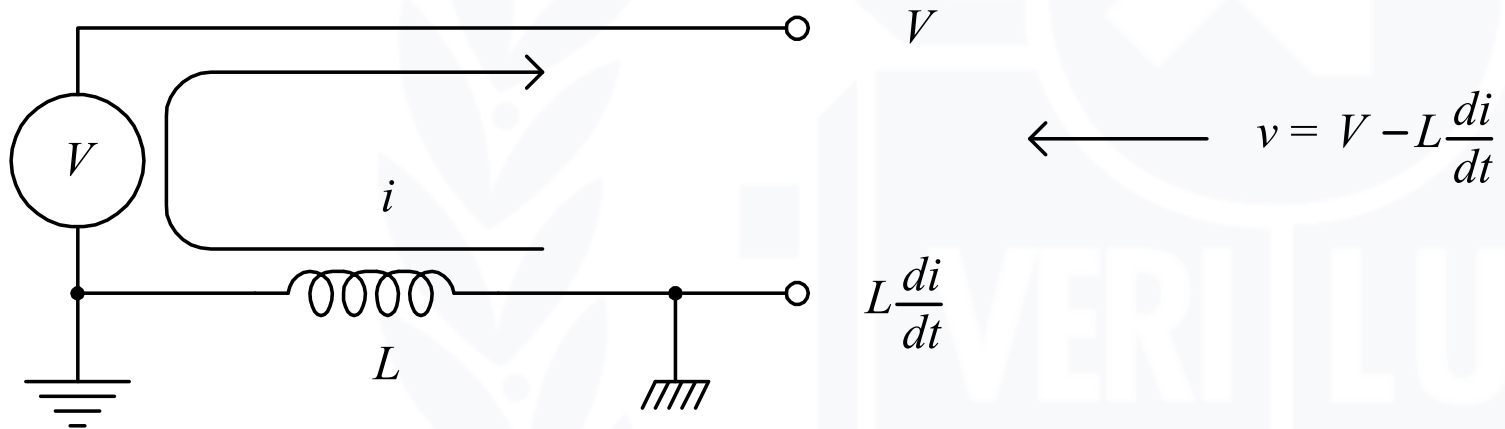

# Low inductance

- Short wire, no bend or loop

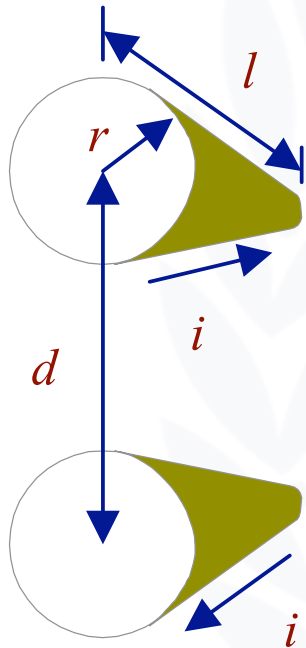


$$L = Kl \ln \frac{d - r}{r}$$




# Signal return path

- VCC and GND are signal return paths!

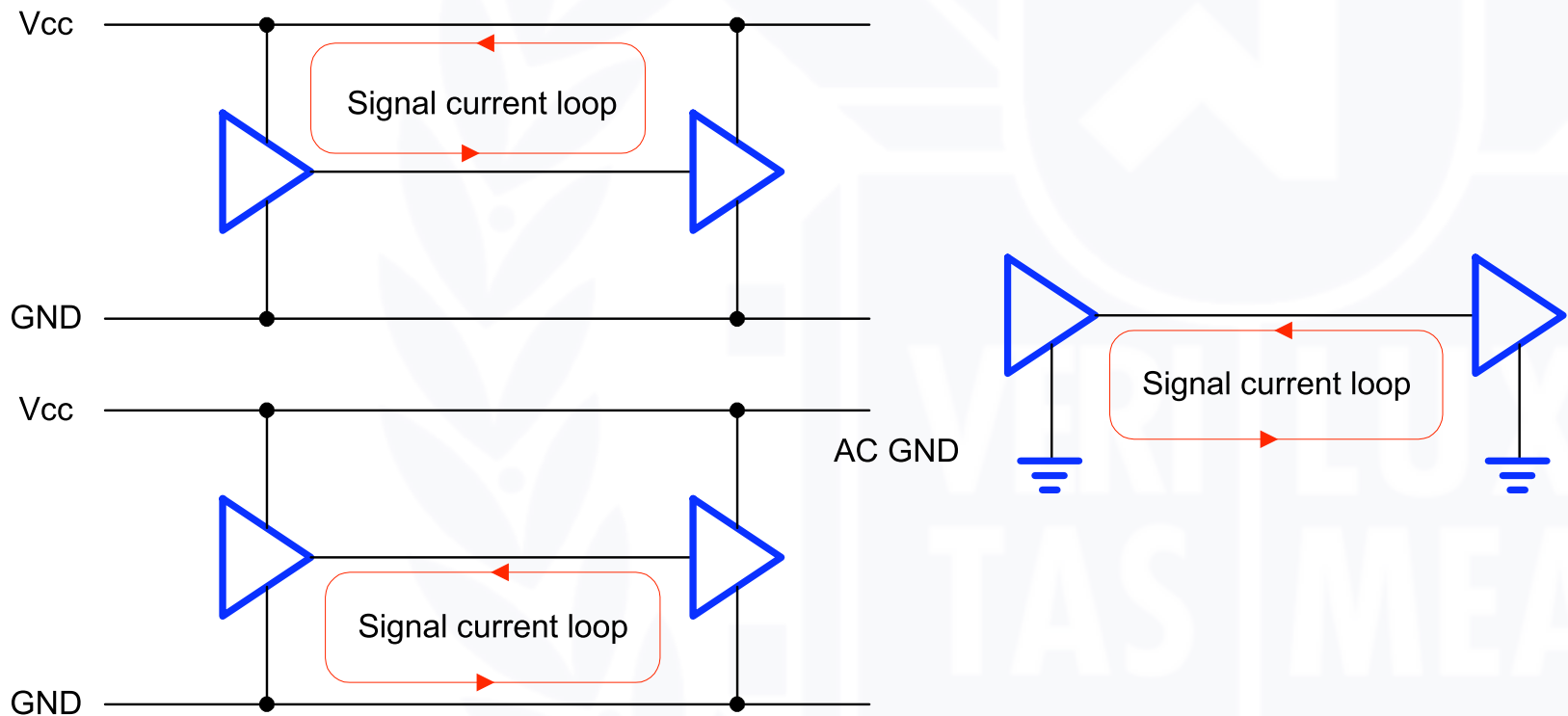

# Minimize signal return path


- Power bus and power plane

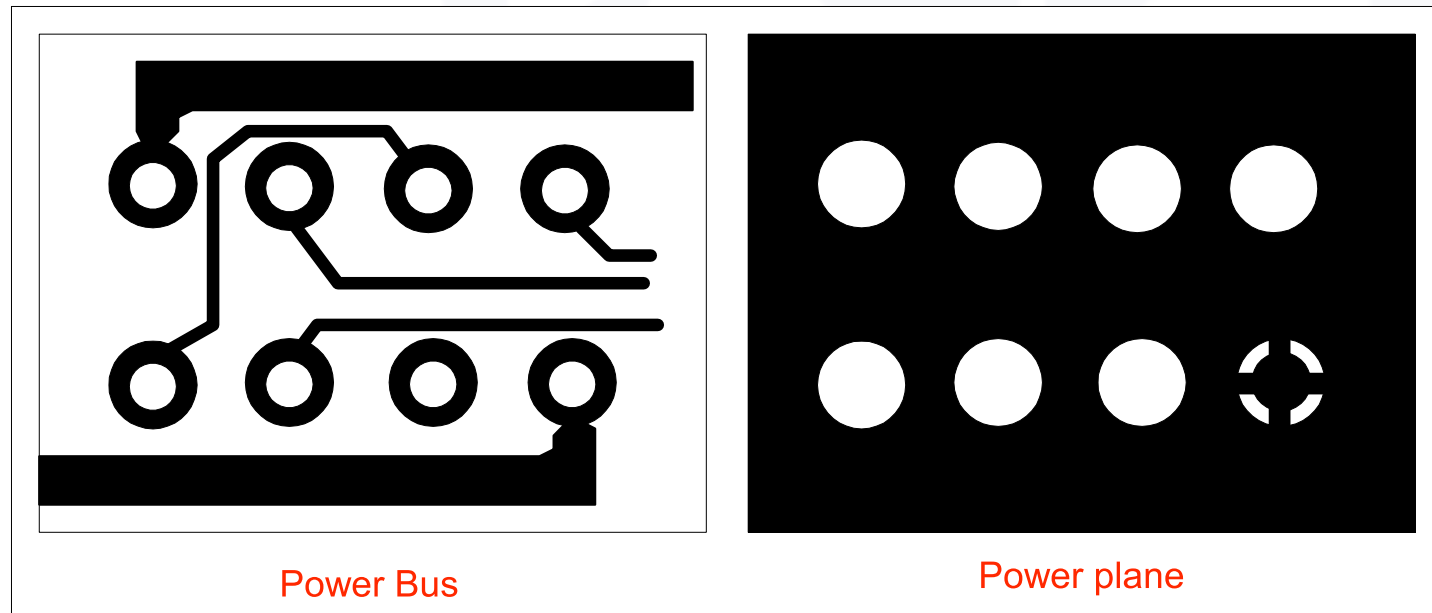

# Power bus


- VCC and GND fingers layout
- Track width?

$$L = Kl \ln \frac{d - r}{r}$$

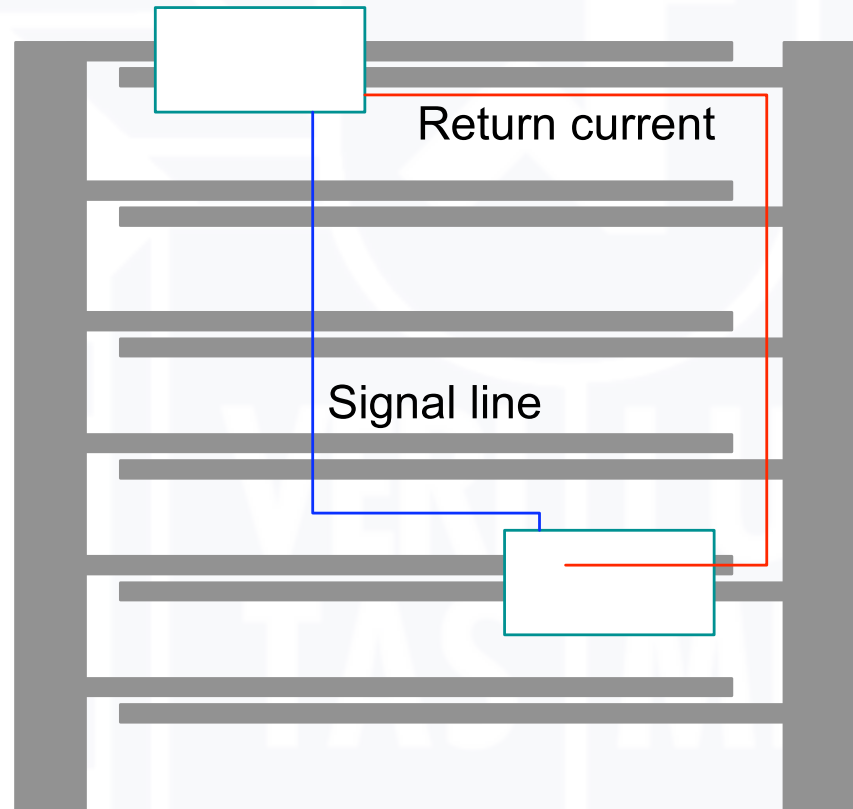

# Power bus (2)


- VCC and GND grid on two layers

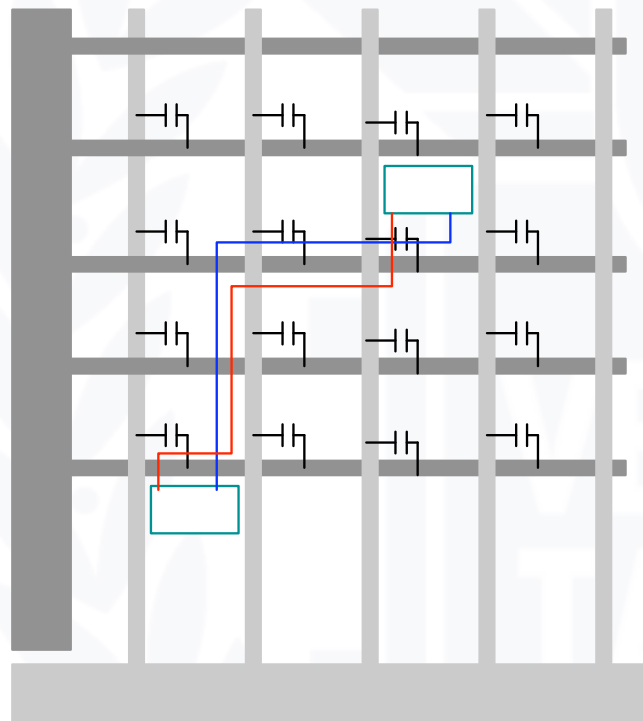



# Solid power planes

- VCC and GND planes
- Ideal for signal return path

VCC Plane

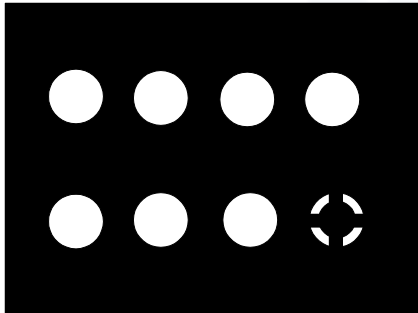


GND Plane

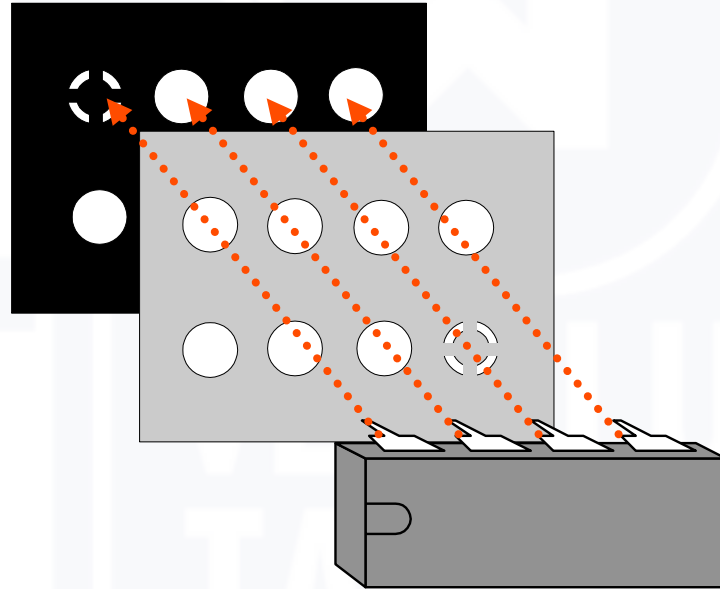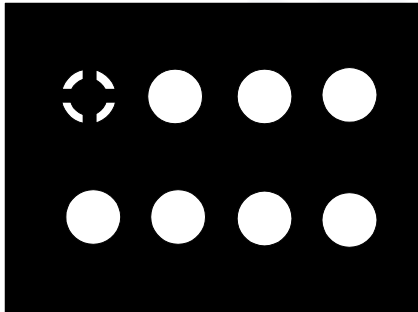


# Solid power planes

## 🔍 Drain pipes

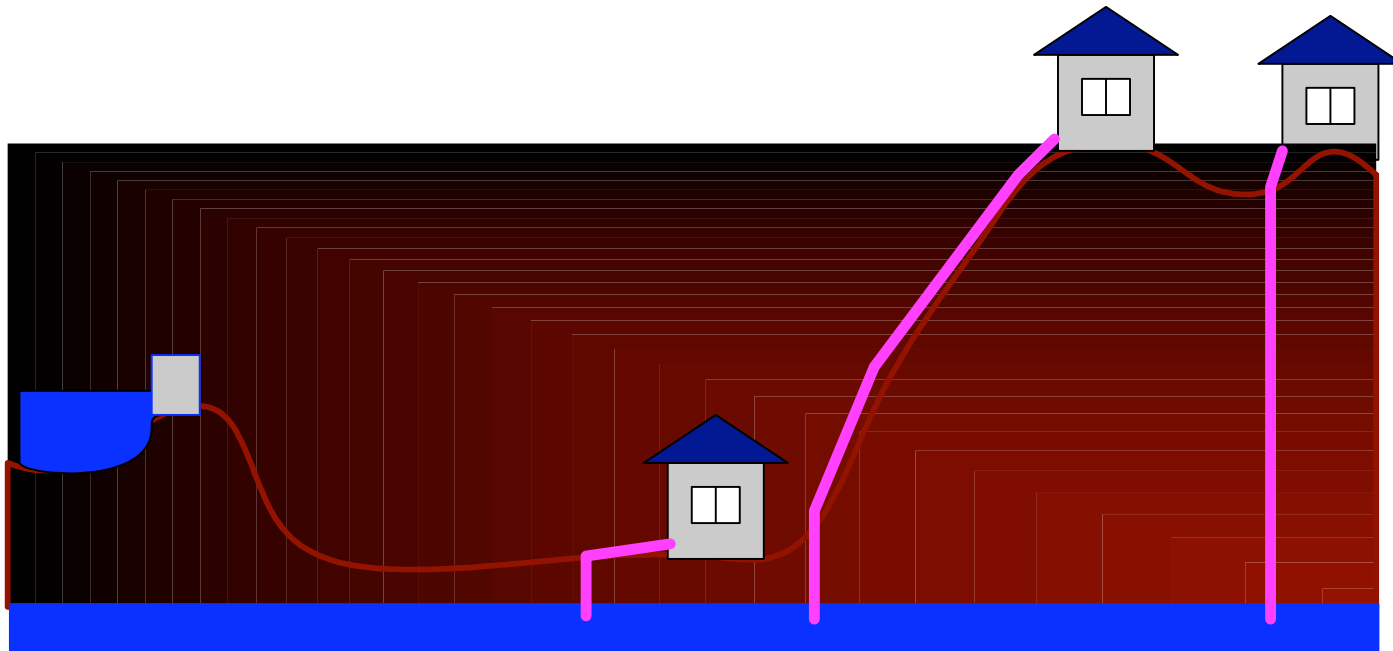



# Bypass capacitor

Water supply

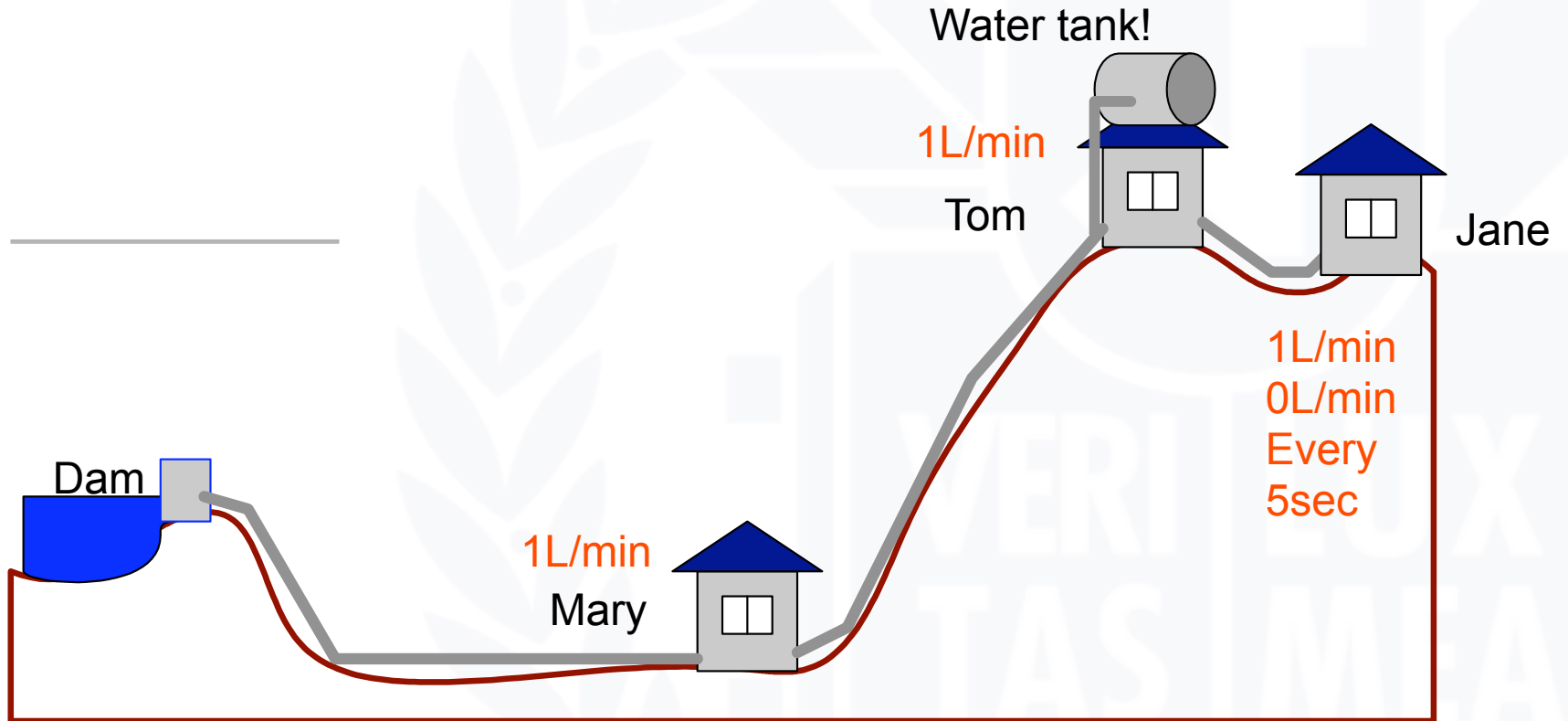
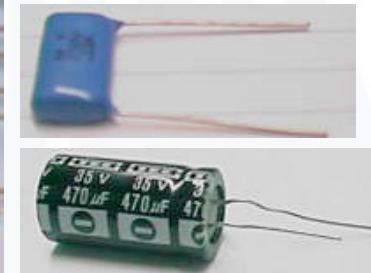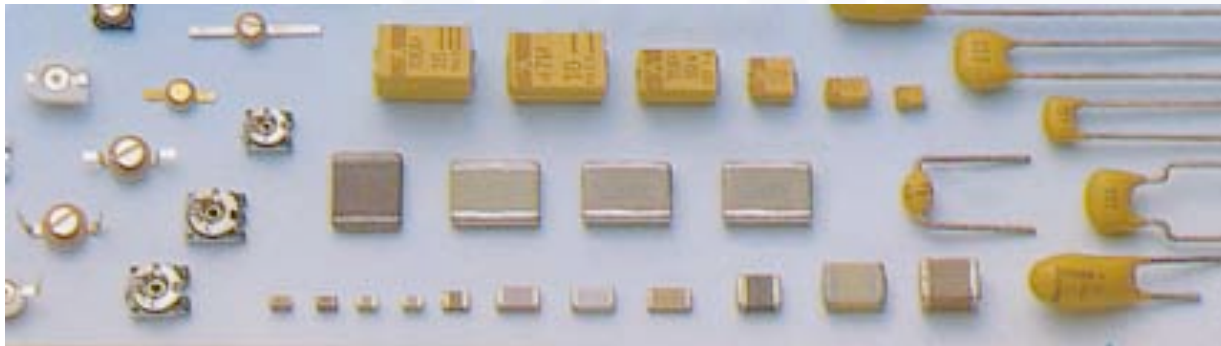
# Bypass capacitor

- Reduce power supply impedance.
- Reduce impedance between VCC and GND.
- Prevent from abrupt current change thus reducing ground bounce.
- Monolithic and chip capacitors





# Bypass capacitor (contd.)

- For digital systems
  - Low equivalent series inductance (ESL) and low equivalent series resistance (ESR) capacitors.



a) Ideal




b) real condition

# Single sided universal PCB

- Use power bus
  - VCC and GND fingers layout
  - As straight as possible
  - Use tin-plated wire
  - Use bypass capacitors
  - RLC, diode and transistor experiments


# Double sided solid GND plane universal PCB

- Use solid GND plane

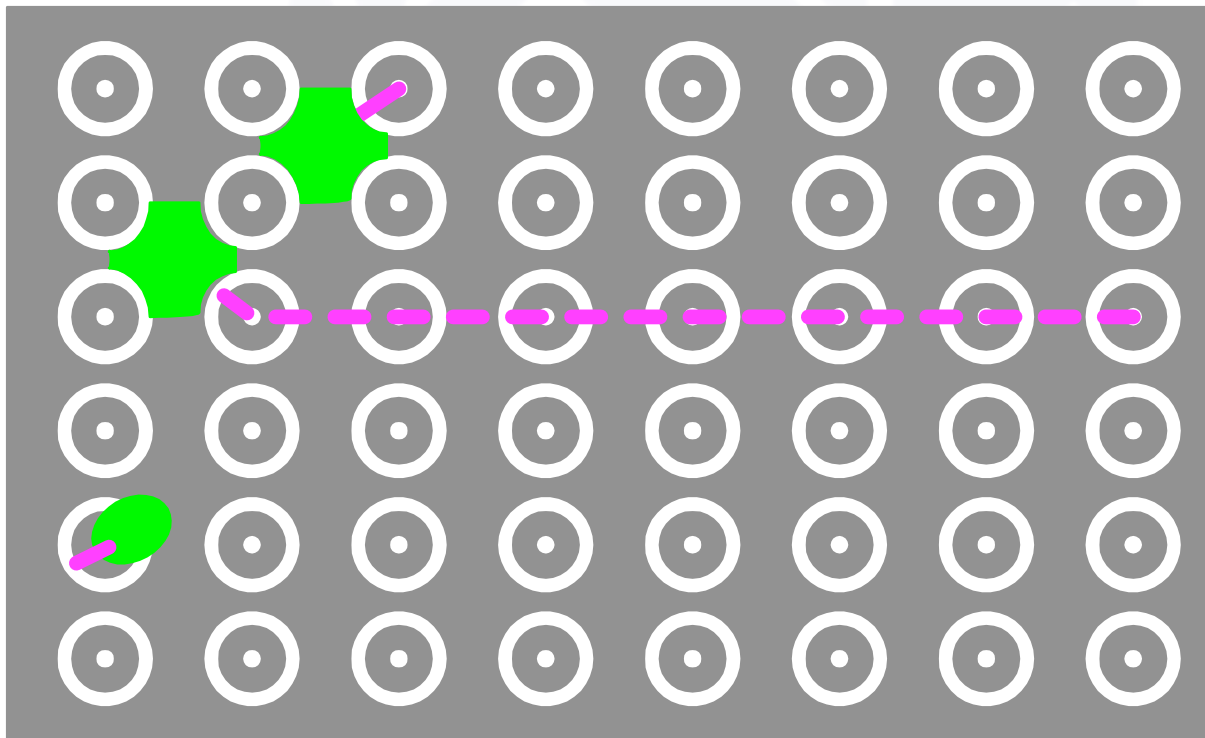

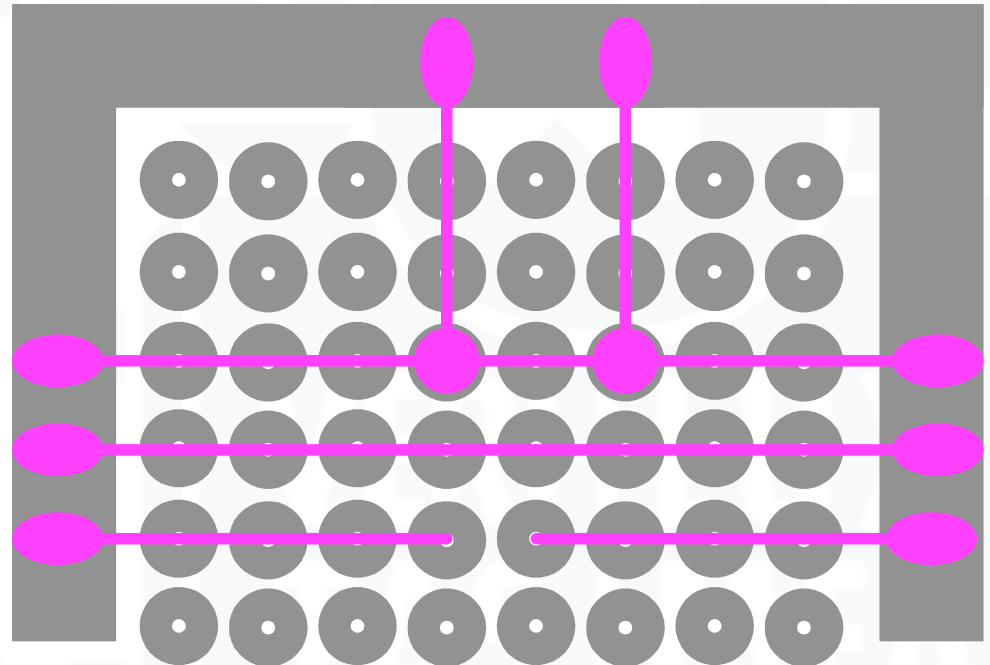
# Double sided solid GND plane universal PCB (contd.)

- Make VCC mesh (grid)
  - Still worse than GND
- Use plenty of bypass capacitors
  - Compensate VCC impedance




# SNUCOM board: component side

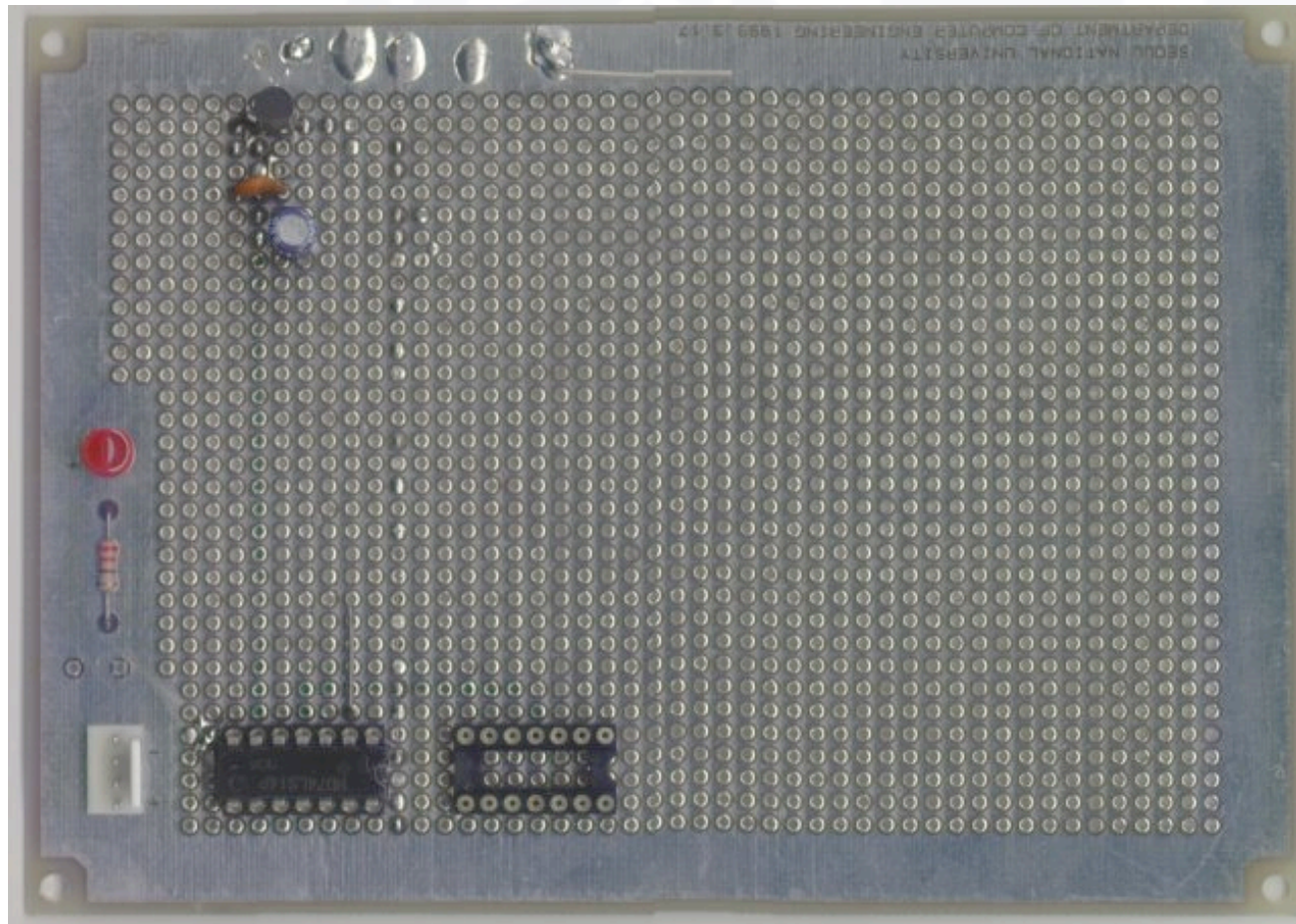




# SNUCOM board: solder side

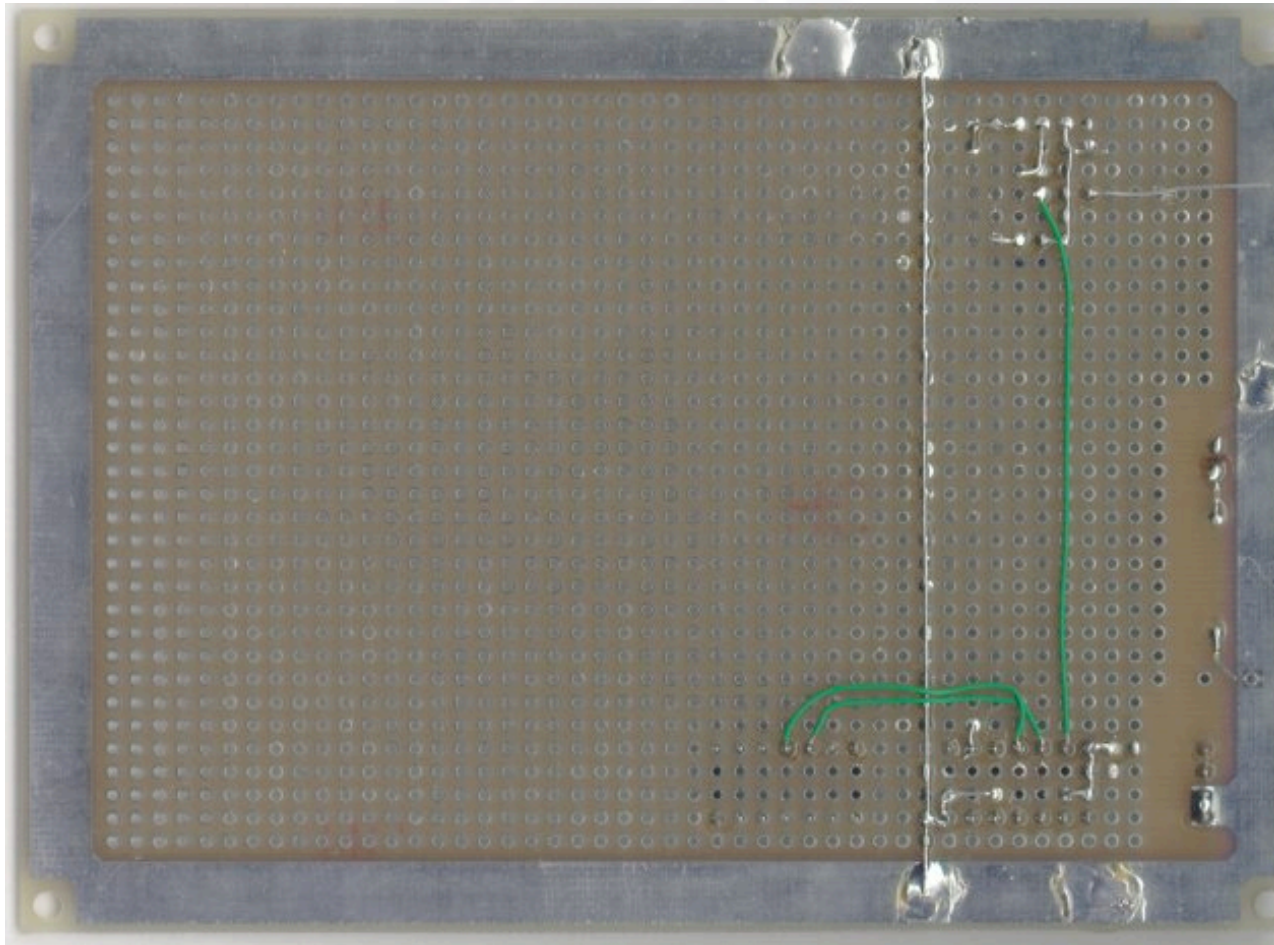

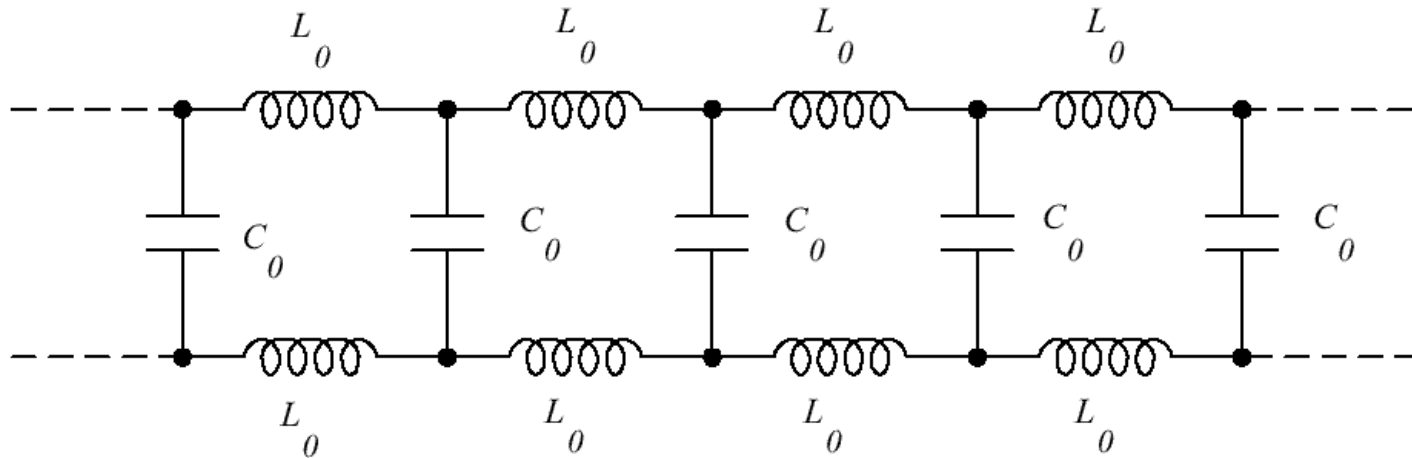
# Controlled impedance line

- Inductance and capacitance are evenly distributed along the length of the line




# Controlled impedance line (contd.)

## ● Stripline and microstripline

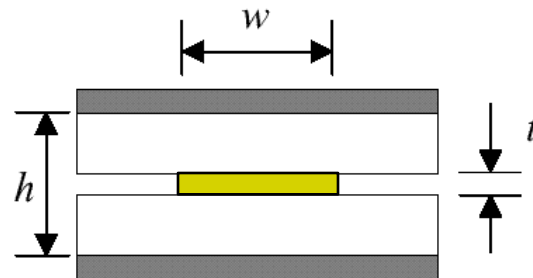

Stripline

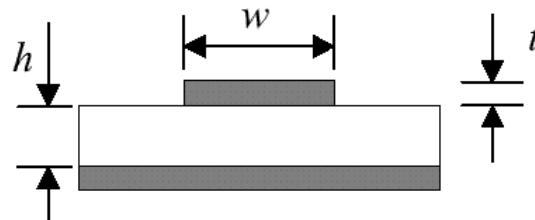

Microstripline



# Controlled impedance line (contd.)

- Coplanar waveguide
  - Often used in RF circuits
  - Often can be seen with copper pour

